

# Antenna Matching for the TRF7960 RFID Reader

John Schillinger


## 1 Introduction

This paper describes the design method for determining an antenna matching circuit. While there are an infinite number of possible impedance matching networks, this application example focuses on a 50-Ω three element match. A three element match is recommended as it allows the designer to select the required antenna quality factor, Q, for the application.

The PCB design used in this application is based on FR4 material,  $\epsilon_r = 4.5$ , with a material thickness of 0.062 inches. The board design is 2 layer design (layer 1 top, & layer 2 bottom), with 2 oz copper.

## 2 Antenna Fabrication

A schematic of a typical antenna circuit is given in [Figure 1](#). The antenna trace width together with the trace spacing, will determine the antenna impedance and Q respectively.

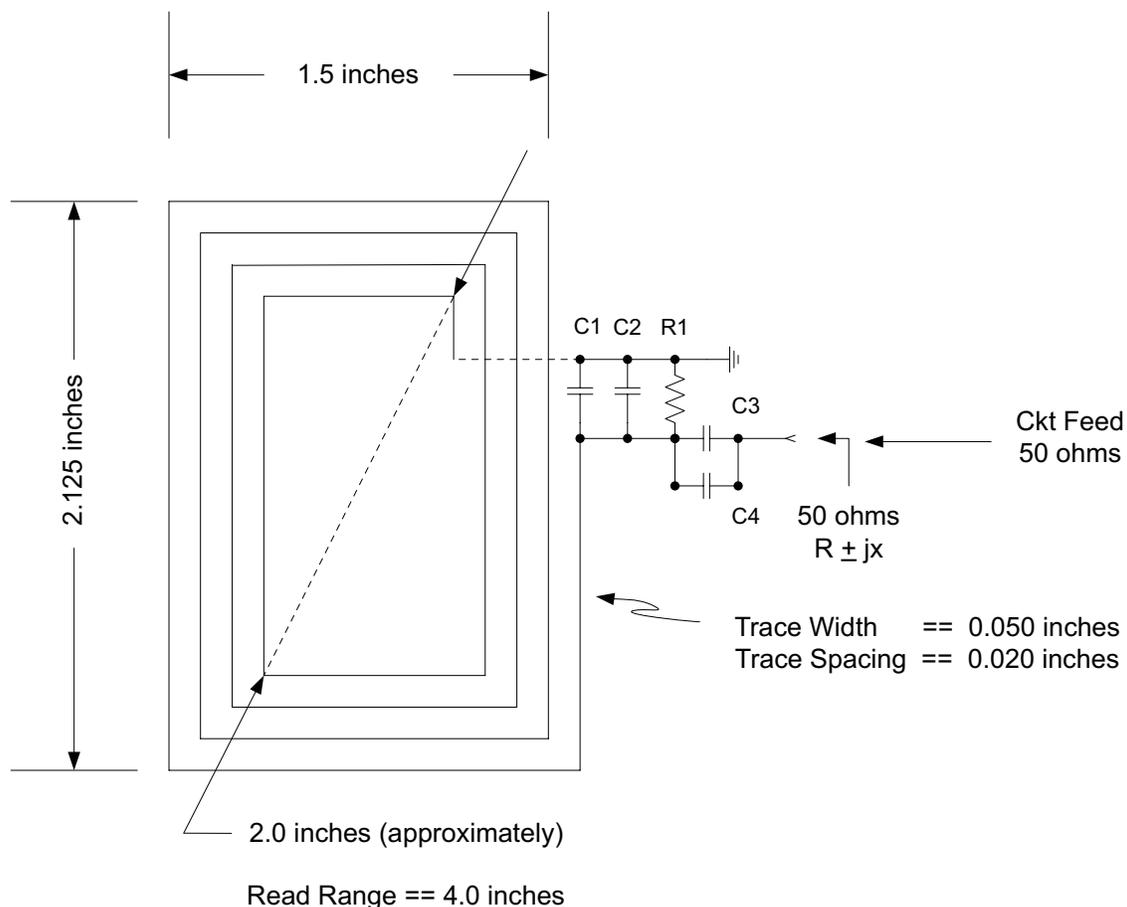

**Figure 1. RFID Antenna (Typical)**

In this application, the antenna is fabricated on the top side of PCB. Some antenna designs will have antenna traces on both top and bottom layers. In either case, it is important to keep ground planes away from antenna traces or elements.

Notice that the antenna drawing (Figure 1) shows a diagonal measurement of approximately 2.0 inches. A rule of thumb is that the expected read range is twice the antenna diagonal measurement.


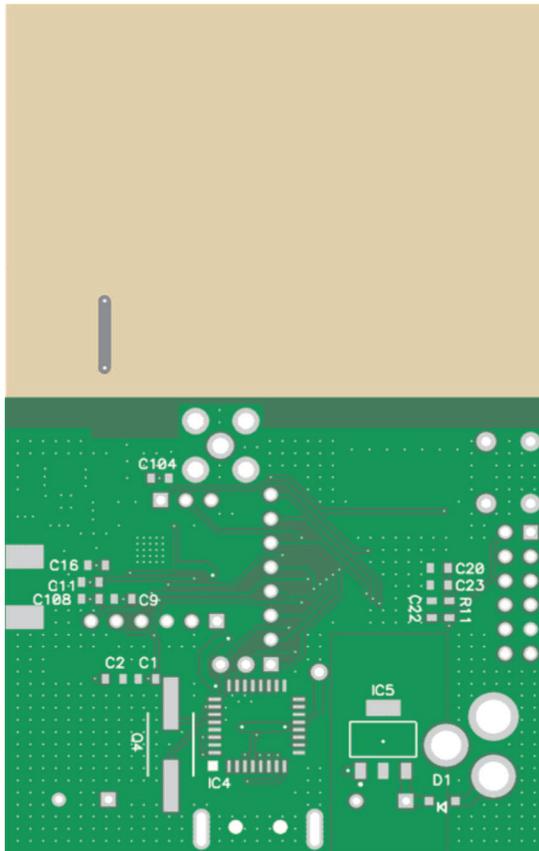


Figure 2. Antenna Bottom Layer

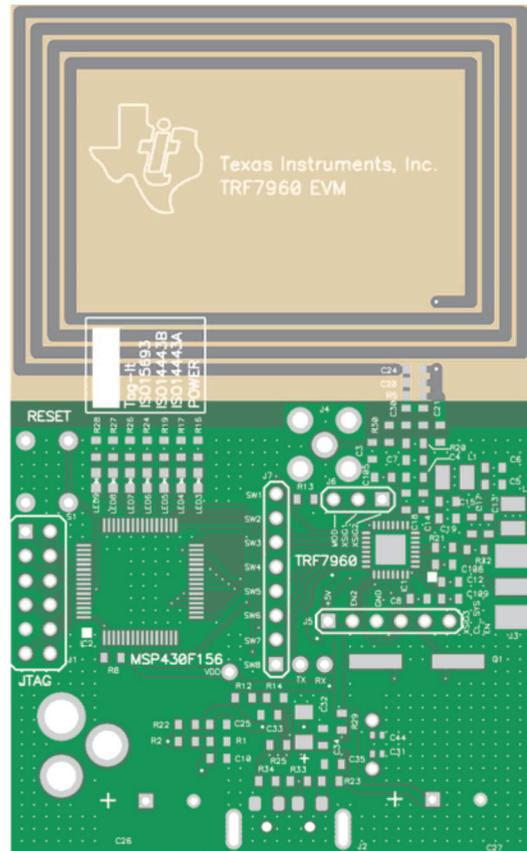

### 3 Antenna Impedance Matching

A three element match is used as it has the added advantage of allowing the circuit Q to be a chosen value.

$$Q = F_0/BW = 13.56 \text{ MHz}/2 \text{ MHz} = 6.78 \quad (1)$$

Where the required operating bandwidth is chosen at 2 MHz.

The first step in impedance matching is calibrating the network analyzer. This is done by connecting a RF test connector on three blank circuit boards, one with a 50 load, second with a short (0-Ω resistor), and third with an open. By using the application board in the calibration, PCB parasitic effects are accounted for.

Following the calibration step, the antenna trace is connected to the test connector as required by 0-Ω resistors. The antenna trace is measured as shown in Figure 4; the resulting measurement is the starting impedance which will be matched to 50 Ω.

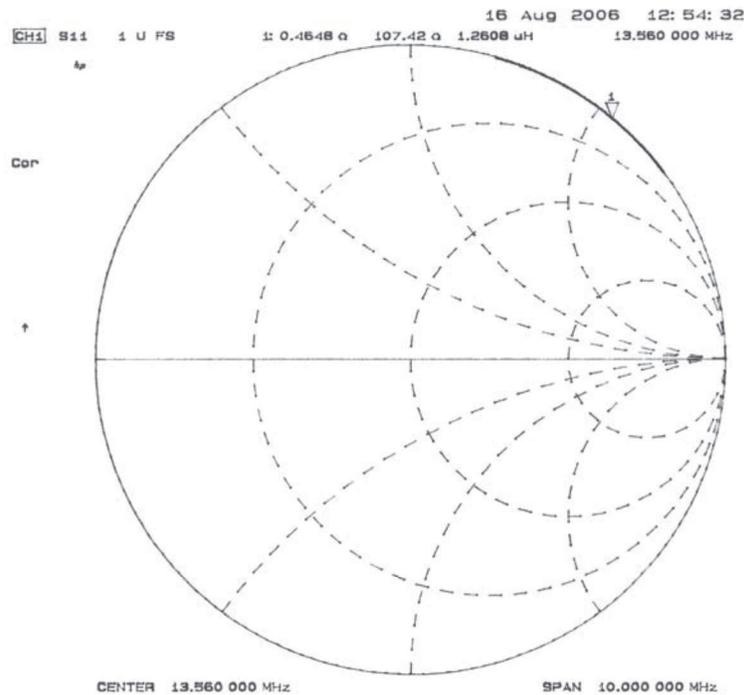


Figure 4. Antenna Impedance = = (0.4648 Ω + j107.42) = = 1.2608 μH

The measured antenna impedance (0.4648 + j107.42) at 13.56 MHz is shown in Figure 4. Note that in this application the antenna impedance is at the Smith Chart's outer limit; or other wise stated the starting impedance is up against the rail. This makes the impedance matching a little more difficult.

A minimum bandwidth (BW) of 2 MHz is chosen in order to accommodate the upper and lower RFID sidebands for various data rates given in ISO15693 & ISO14443 A/B. Hence the approximate resistor value needed is determined as follows:


$$Q = F_0/BW = 13.56 \text{ MHz}/2 \text{ MHz} = 6.78 \quad (2)$$

$$Q = R_p/X_L = R/2 \times \pi \times 13.56 \text{ MHz} \times 1.2608 \text{ μH} = R/107.42 \quad (3)$$

Note that the  $X_L$  value is the same as the measured Smith Chart value (107.42) from Figure 4.

$$R_p = Q \times X_L = 6.78 \times 107.42 = 728 \text{ Ω} \quad (4)$$

Figure 5 is a Smith Chart impedance matching simulation.

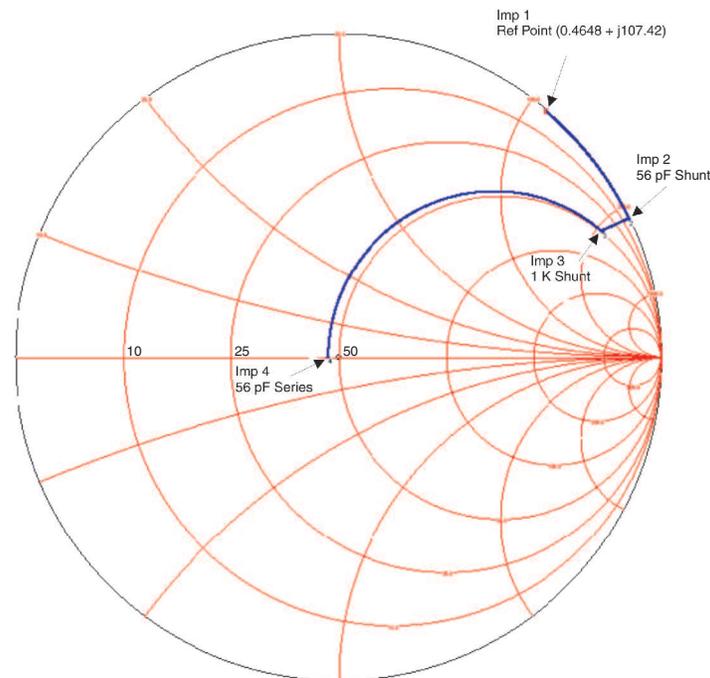

**Figure 5. Smith Chart Impedance Match Simulation**

The measured impedance from [Figure 4](#) is shown in [Figure 5](#) as Imp 1. A shunt 56-pF capacitor rotates the impedance to Imp 2. Next a shunt resistor (which sets the antenna Q or BW), rotates the impedance from Imp 2 to Imp 3; where the impedance is now on the 50-Ω circle. The final matching element is a 56-pF capacitor, which rotates the impedance from Imp 3 to Imp 4 ( $46.6 + j0.3$ ). This capacitor is split into two parallel caps (47 pF + 10 pF) to allow fine tuning of the antenna frequency while also reducing component parasites.

Note earlier the shunt resistor was calculated to be 728 Ω whereby it is now rounded to up to 1.0 KΩ in order to yield a match with standard capacitor values.

Final circuit values for the antenna circuit given in [Figure 1](#) are as follows:

C1 = = 56 pF


C2 = = DNP (Do Not Place)

R1 = = 1 .0 KΩ


C3 = = 47 pF

C4 = = 10 pF

## 4 Antenna Performance

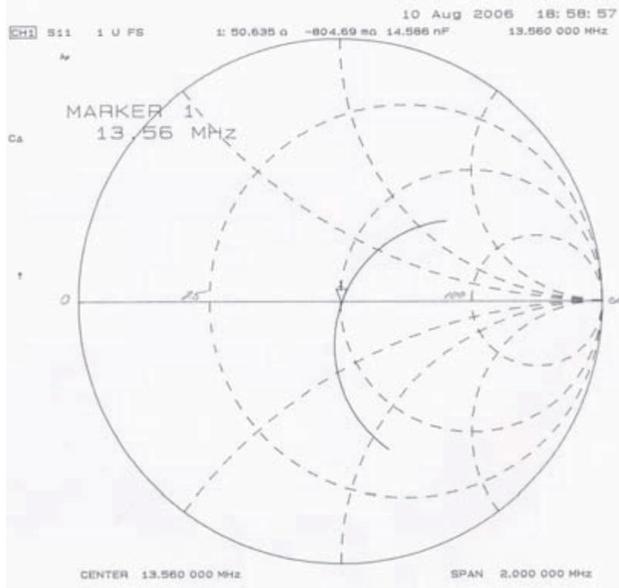


**Figure 6. Smith Chart**  
 $(50.635 - j804.67) = 14.586 \text{ nF}$

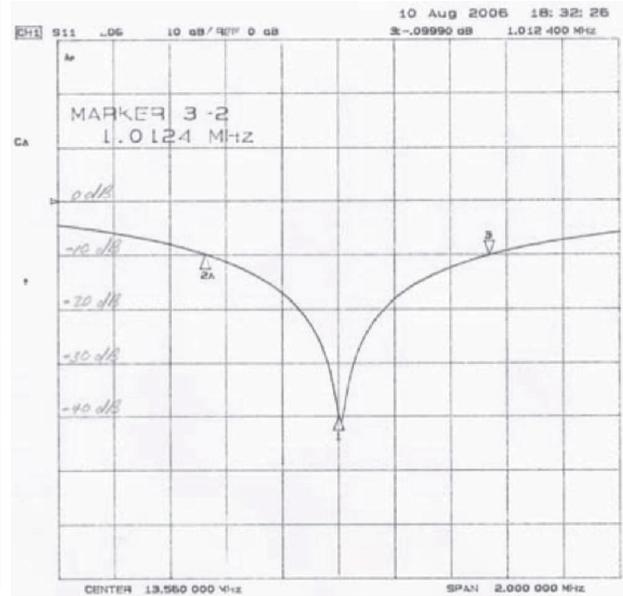


**Figure 7. Return Loss**  
 (RL = 40 dB at 13.56 MHz)

Note that [Figure 7](#) shows a 10 dB return loss over a 1.0124-MHz BW (Mkr 3-2). A rule of thumb is that the antenna 3-dB BW is twice the 10-dB return loss bandwidth. Applying the rule to this application would yield an antenna bandwidth of 2.248 MHz.

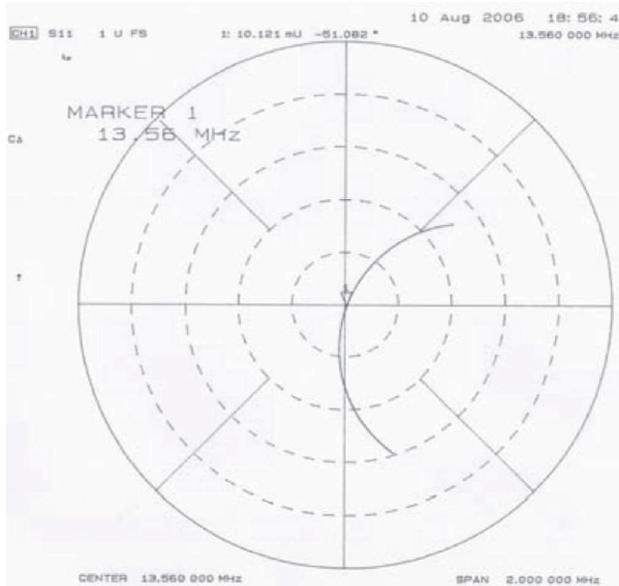

**Figure 8. Polar Plot**

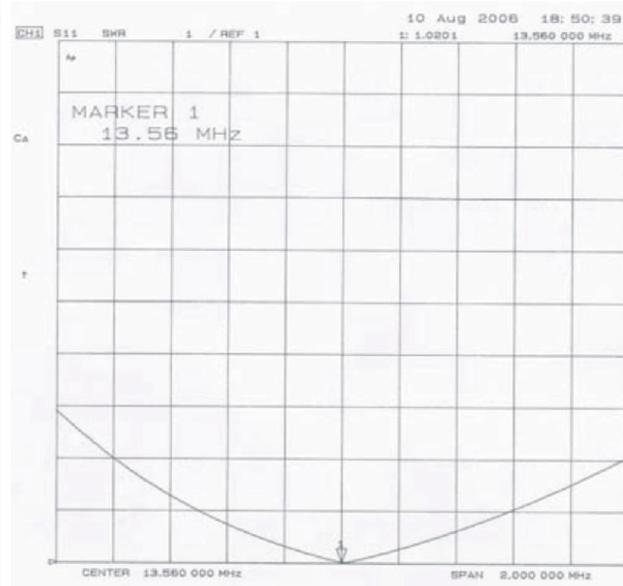

**Figure 9. VSWR Plot**

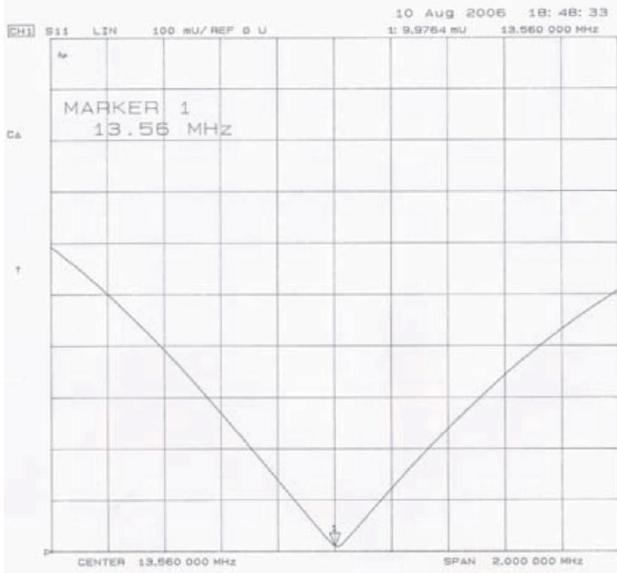


Figure 10. Linear Plot



Figure 11. Phase Plot

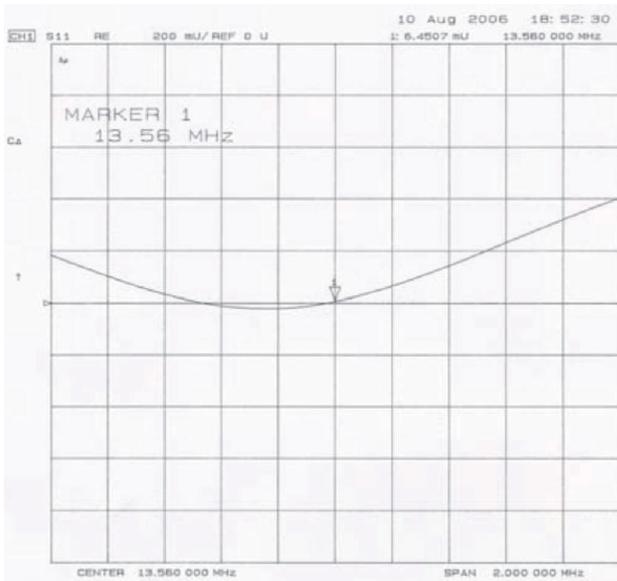


Figure 12. Real Part



Figure 13. Imaginary Part

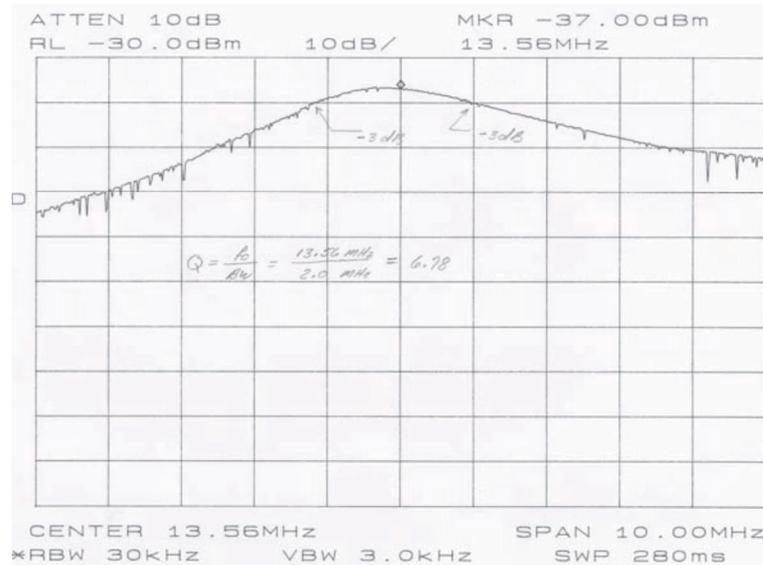


Figure 14. Measured Antenna Bandwidth and Q

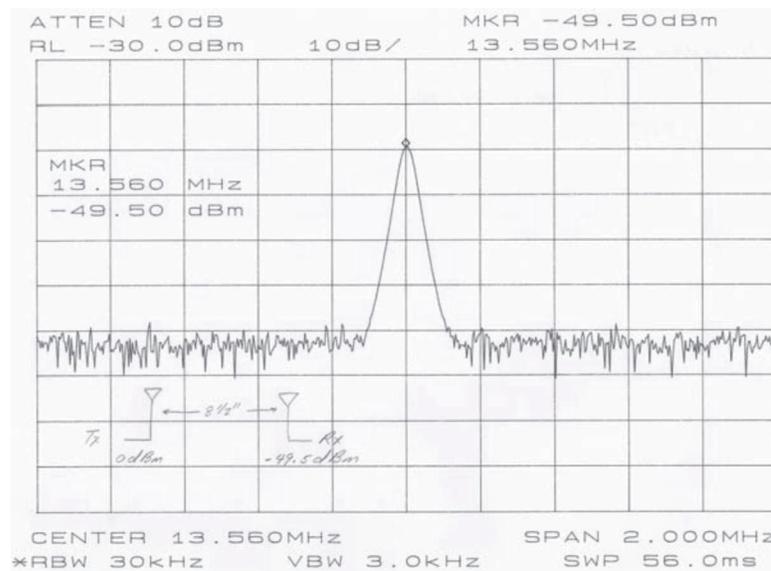


Figure 15. Antenna Transmission Test

As a final test to ensure the antenna elements will radiate, a test set up was established. A 0-dBm CW signal is applied to the Tx antenna; the Rx antenna is placed 8.5 inches from the Tx antenna (the width of a standard piece of office paper). The output from the Rx antenna is measured on a spectrum analyzer which shows a -49.5-dBm signal level. Both Tx & Rx antenna are PCB RFID reader antennas.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)